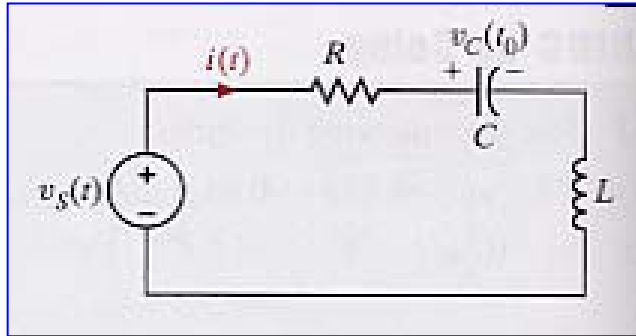


RLC Transient Response




Second-order Circuits



Second-order series RLC circuit

$$Ri(t) + \frac{1}{C} \int_{t_0}^t i(x) dx + v_C(t_0) + L \frac{di(t)}{dt} = v_S(t)$$
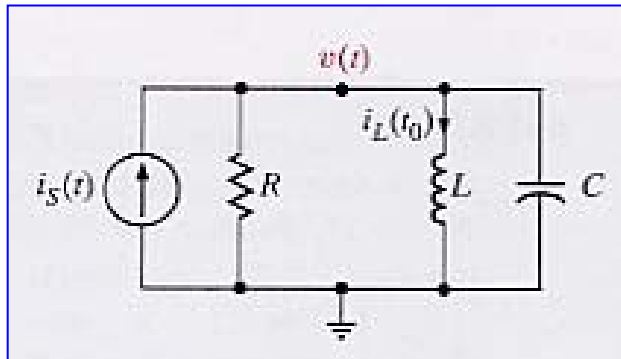
$$\Rightarrow L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{i(t)}{C} = \frac{dv_S(t)}{dt}$$



Second-order parallel RLC circuit

$$\frac{v(t)}{R} + \frac{1}{L} \int_{t_0}^t v(x) dx + i_L(t_0) + C \frac{dv(t)}{dt} = i_S(t)$$

$$\Rightarrow C \frac{d^2 v(t)}{dt^2} + \frac{1}{R} \frac{dv(t)}{dt} + \frac{v(t)}{L} = \frac{di_S(t)}{dt}$$

General Solution

Differential equation

Homogeneous solution
(zero input response)

+

Particular solution
(zero initial state response)

가
Initial value response

initial value가
response

General second-order differential equation

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2x(t) = A$$

$$\left\{ \begin{array}{l} x(t) = x_p(t) : \text{particular solution for } \frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2x(t) = A \\ x(t) = x_c(t) : \text{homogeneous solution for } \frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2x(t) = 0 \end{array} \right.$$


$$\Rightarrow \text{General solution} : x(t) = x_p(t) + x_c(t)$$



Particular Solution

$$\frac{d^2 x_p(t)}{dt^2} + a_1 \frac{dx_p(t)}{dt} + a_2 x_p(t) = A \Rightarrow x_p(t) = \frac{A}{a_2} \quad \therefore x(t) = \frac{A}{a_2} + x_c(t)$$

Homogeneous Solution

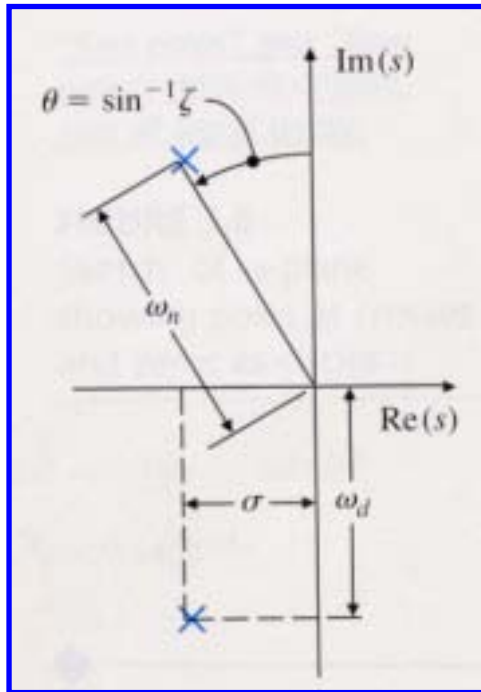

<s-domain plot of roots>

$$\frac{d^2 x_c(t)}{dt^2} + a_1 \frac{dx_c(t)}{dt} + a_2 x_c(t) = 0 \Rightarrow \frac{d^2 x_c(t)}{dt^2} + 2\zeta\omega_0 \frac{dx_c(t)}{dt} + \omega_0^2 x_c(t) = 0$$

Assume $x_c(t) = Ke^{st}$

then $s^2 Ke^{st} + 2\zeta\omega_0 s Ke^{st} + \omega_0^2 Ke^{st} = 0$ ($a_1 = 2\zeta\omega_0, a_2 = \omega_0^2$)

$\Rightarrow \underline{s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0}$: characteristic equation

roots : $s = -\zeta\omega_0 \pm j\omega_0\sqrt{1-\zeta^2} = -\sigma \pm j\omega_d$ $\begin{cases} \sigma = \zeta\omega_0 \\ \omega_d = \omega_0\sqrt{1-\zeta^2} \end{cases}$

- ζ : damping ratio() - 가
- $\zeta > 1$: overdamping() -
- $\zeta = 1$: critical damping() - 가
- $\zeta < 1$: underdamping() - exponential envelope

- ω_0 : undamped natural frequency
 - $\omega_0 = 0$, $s = j\omega_0$ (purely imaginary) sine wave

Homogeneous Solution - continue

two roots : $s_1 = -\zeta\omega_0 + j\omega_0\sqrt{1-\zeta^2}$, $s_2 = -\zeta\omega_0 - j\omega_0\sqrt{1-\zeta^2}$

then $x_c(t) = K_1e^{s_1t} + K_2e^{s_2t}$ and K_1, K_2 is obtained from initial conditions

i) $\zeta > 1$: overdamping. s_1, s_2 are real and unequal.



$$\underline{x_c(t) = K_1e^{-(\zeta\omega_0 - \omega_0\sqrt{\zeta^2 - 1})t} + K_2e^{-(\zeta\omega_0 + \omega_0\sqrt{\zeta^2 - 1})t}}$$

ii) $\zeta < 1$: underdamping. s_1, s_2 are complex conjugate


$$\underline{x_c(t) = e^{-\zeta\omega_0 t} (A_1 \cos \omega_0\sqrt{1-\zeta^2}t + A_2 \sin \omega_0\sqrt{1-\zeta^2}t)}$$

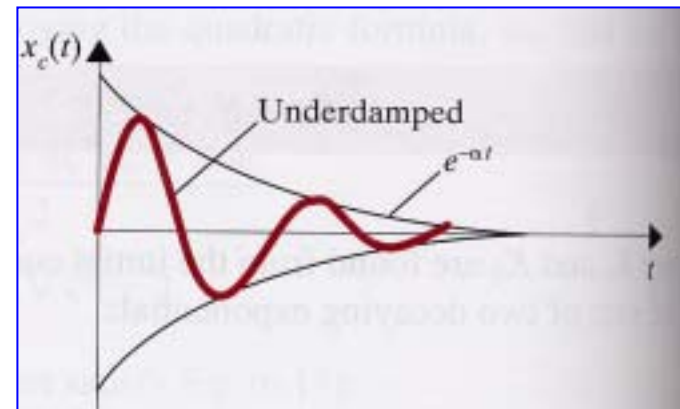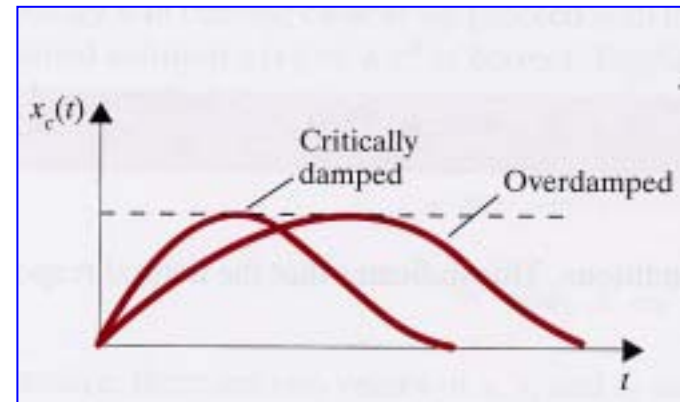iii) $\zeta = 1$: critical damping. $s_1 = s_2 = -\omega_0$

$$\underline{x_c(t) = B_1e^{-\zeta\omega_0 t} + B_2te^{-\zeta\omega_0 t}}$$



Example : Series RLC

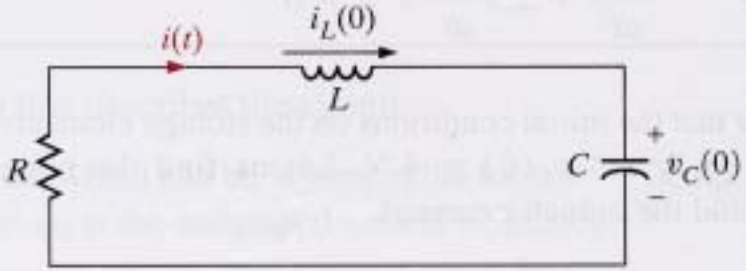

$$R=6\text{ohm}, L=1\text{H}, C=0.04\text{F}, i_L(0)=4\text{A}, v_C(0)=-4\text{V}$$

i) second-order differential equation

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{i(t)}{LC} = 0 \quad \longrightarrow \quad \frac{d^2i(t)}{dt^2} + 6 \frac{di(t)}{dt} + 25i(t) = 0$$

ii) Characteristic equation

$$s^2 + 6s + 25 = 0 \Rightarrow s_1 = -3 + j4, s_2 = -3 - j4 : \textit{underdamping}$$

iii) General solution

$$i(t) = K_1 e^{-3t} \cos 4t + K_2 e^{-3t} \sin 4t$$

iv) Applying initial conditions

$$i(0) = 4 = K_1$$

$$\text{From KVL, } Ri(0) + L \frac{di(0)}{dt} + v_C(0) = 0 \Rightarrow \frac{di(0)}{dt} = -20$$

$$\frac{di(0)}{dt} = -3K_1 + 4K_2 = -20 \Rightarrow K_2 = -2$$

v) Final response

$$i(t) = 4e^{-3t} \cos 4t - 2e^{-3t} \sin 4t$$

$$\text{From KVL, } v_C(t) = -4e^{-3t} \cos 4t + 22e^{-3t} \sin 4t$$

